


ENR 325 Assignment #1.5

Due: 9/5/25 10:00 pm

1. Install this game:


<https://sebastian.itch.io/digital-logic-sim>

Build the following I/O of a NAND gate:

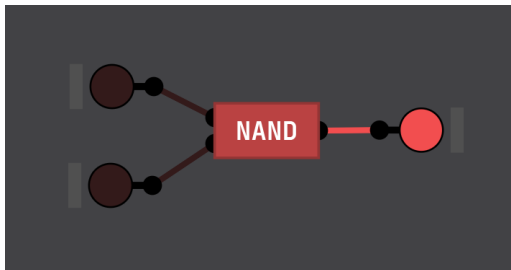

And use one sentence (or one truth table) to tell what it does. Reporting as one slide.

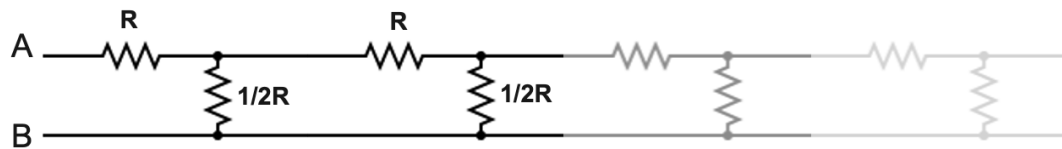2. Let's do one more infinite resistor (<https://what-if.xkcd.com/113/>):




To get: equivalent resistor between point A and B, if the ladder go infinite.


Do it two ways:

First modify the quadratic equation and get the answer (Sam, you can skip this).

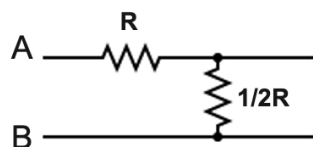Second, do the circuit analysis on level 1 (R1):



level 2 (R2):

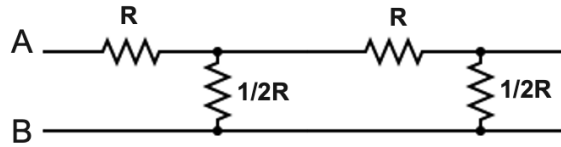

Level 3 (R3)... until level N.

Then derive the quadratic equation based on $R(N)=R(N-1)$, when $N \rightarrow \infty$.

3. Let's do one more puzzle from the MIT open course:

Problem 1-3: You are given a black box with three terminals, as shown below. The box is known to contain five 1-ohm resistors.



Using an ohm-meter, you measure the resistance between the terminals to be the following:

A - B: 1.5 ohms

B - C: 3 ohms

A - C: 2.5 ohms

Determine the configuration of the five resistors inside the box.

I use <https://www.circuit-diagram.org/> to draw circuit diagram. But you can use anything else!